

# **Transmission Lines**

## **Topics of the course**

- **Limitation of the circuit theory**
- **Definition & types of transmission lines (TL)**
- **Primary TL parameters**
- **The distributed-element model of TL**
- **The first order equations (and second) of TL**
- **Derivation of power equation**
- **Steady-state TL equations.**
- **Equivalent TL equations**
- **Semi-infinite TL**
- **Heaviside TL conditions**

## Limitations of the circuit theory

At low frequencies, **circuit theory** is generally adequate to explain the behavior of collections of electronic components interconnected by wires. Such circuits are modeled using: **lumped circuits**.

As frequency increases, the circuit approximation becomes progressively **less good**, for a number of reasons:

- the energy stored in **reactive components** is held in the space around the components, and different components can have "fields" which overlap;
- **wires** are also reactive components which store energy;
- the division of the circuit into separate reactive components interconnected by non-reactive "wires" is only an approximation.

## Lumped circuits

- Assumes that the entire circuit is at a single point (lumped).
- This means that circuit component dimensions are unimportant.
- Voltage & current do not vary across the component.
- Voltage applied at one point, the rest of the circuit reacts instantly.
- We don't have to consider travel time of the signal across components.
- Typical lumped elements are resistors, capacitors, inductors.

## The Lumped-Element Model



- **Lumped-element** model for the entire transmission as seen from A-A' and B-B':

$$i_1 = i_2 \quad (\text{KCL})$$

$$u_1 = u_2 \quad (\text{KVL})$$

**Valid only if**

$l$  (length of the line)  $\ll \lambda$  (wavelength of the signal)

## Light speed


But .....the speed of light is finite and electromagnetic signals (**in free space**) travel at the light speed.

$$c_0 = 3 \times 10^8 \text{ m/sec}$$

In practical transmission systems the actual speed of the signal is determined by **electrical and magnetic properties** of the surrounding media and the **geometry** of the conductors.

So what does a distributed circuit look like?

## A Long Wire!

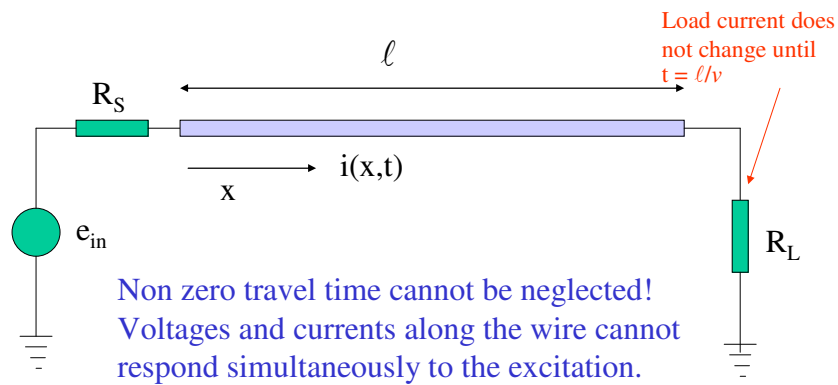

## When do we use lumped/distributed analysis?

For steady state sinusoidal applications we can look at the **one way propagation delay** time  $t_d$ .

Say we have an excitation  $e_{in} = E \cdot \sqrt{2} \cdot \sin(\omega t)$

Then the voltage at a distance of  $\ell$  is delayed by  $t_d = \ell/v$

This voltage is:

$$u_\ell(t) = E \cdot \sqrt{2} \cdot \sin[\omega(t - t_d)]$$

$$= E \cdot \sqrt{2} \cdot \sin\left[\omega t - 2\pi \frac{t_d}{T}\right]$$

$T = 1/f$   
= period

**The delay is dependent with the frequencies !!**

## Two options

### 1. $t_d \ll T$

Then voltage at  $\ell$  is almost the same as the input voltage.

- treat the line as a **lumped system**.

### 2. $t_d$ comparable to $T$

In this case the voltage down the line can be quite different e.g. at  $t_d = 0.5T$ ,  $u_\ell = -E_{in}$  – **distributed system**.

#### Rules:

Use lumped analysis when:

- $t_d < 0.1T$ , or more stringently when  $t_d < 0.01T$  or *equivalent*
- the wavelength of the electromagnetic signal is comparable with the geometric length of the line:

$$\lambda = c \cdot T = \frac{c}{f} = \frac{3 \times 10^8}{f} [m]$$

## Maximum lengths for lumped applications

Application	Frequency	Wavelength $\lambda = \frac{3 \times 10^8}{f}$	Max length (based on $t_d = 0.01T$ )
Power Transmission	50 Hz	6.000 km	60 km
Telephone	1 kHz	300 km	3 km
TV	150 Mhz	2 m	2 cm
Radar/Microwave	10 GHz	3 cm	0.3 mm
Visible light	$5 \times 10^{14}$ Hz	600 nm	6 nm

## Introduction

The term transmission line is usually reserved for structures that are at least a significant fraction of a wavelength in length and have uniform electromagnetic properties along their length.


Examples are as follows:

- **coaxial lines:** flexible, semi flexible or rigid with solid insulation, perforated insulation or air-spaced;
- **parallel pair of conductors:** parallel wires (air-spaced, insulated); parallel tracks on an insulating substrate;
- **strip-line:** microstrip (in microwave integrated circuits): conducting strips insulated from a conducting ground plane;
- **waveguides:** hollow metal pipes (commonly of rectangular cross-section).


## Main remarks about TL

- **Definition:**  
Structures used to transmit energy or signal in the form of guided-wave electromagnetic fields from one place to another.
- **Modeling:**  
Distributed-element model  
Electromagnetic model (Maxwell equations)
- **Key Concepts:**  
Waves and properties


## Different Types of Transmission Lines

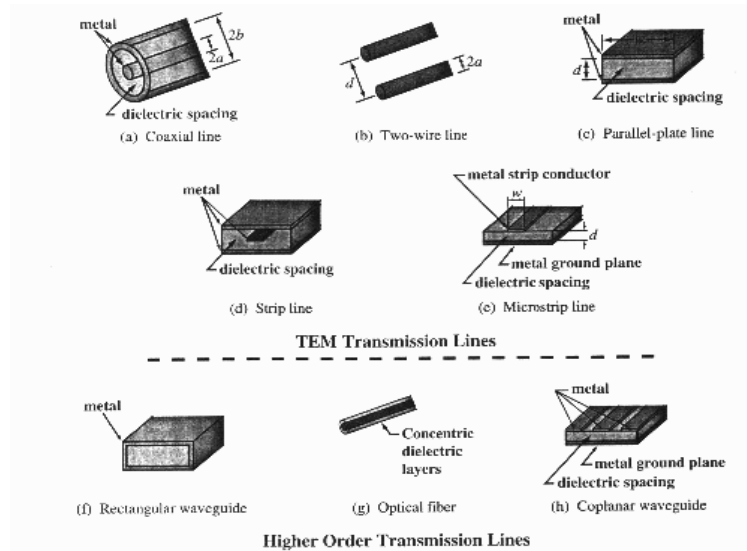

## Types of Transmission lines (cont)

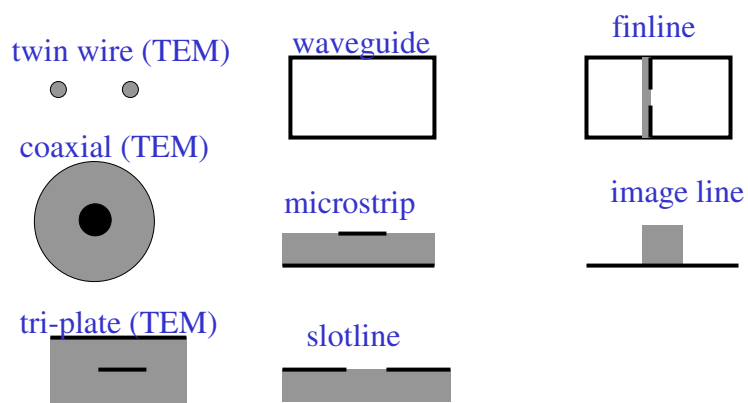


## The Distributed-Element TL Model

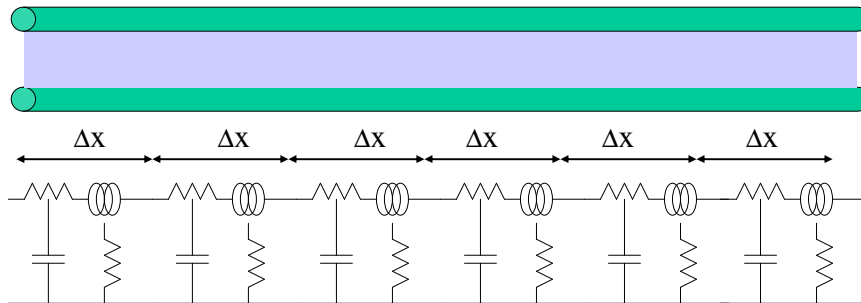

1. Divide the entire transmission line into segments with length  $\Delta x \ll \lambda$
2. For each segment, postulate the lumped elements related to the **series resistance**, the **parallel capacitance**, the **series inductance**, and the **parallel conductance**.
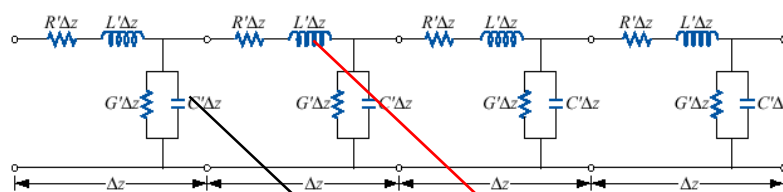
## Distributed element-model

Inductance and Capacitance are the most important parameters.



The current in the line sets up a field and induces a voltage  $\left( L_0 \frac{di}{dt} \right)$

The capacitance exists between the lines.

Both  $L_0$  &  $C_0$  are distributed along the line.

Both are not perfect, some attenuation ( $R_0$  &  $G_0$ ) always exists.



## The primary TL parameters


Any (two-wire) transmission line has four fundamental electrical parameters. They are also called primary line parameters (constants):

- $R_0$ , the series resistance:  $R_0 = \lim_{\Delta x \rightarrow 0} \frac{\Delta R}{\Delta x}$
- $L_0$ , the series inductance:  $L_0 = \lim_{\Delta x \rightarrow 0} \frac{\Delta L}{\Delta x}$
- $C_0$ , the shunt capacitance:  $C_0 = \lim_{\Delta x \rightarrow 0} \frac{\Delta C}{\Delta x}$
- $G_0$ , the shunt conductance (or leakage):  $G_0 = \lim_{\Delta x \rightarrow 0} \frac{\Delta G}{\Delta x}$

In general, these lines parameters are referred to a loop or pair of wires of fixed length or per unit length of line.
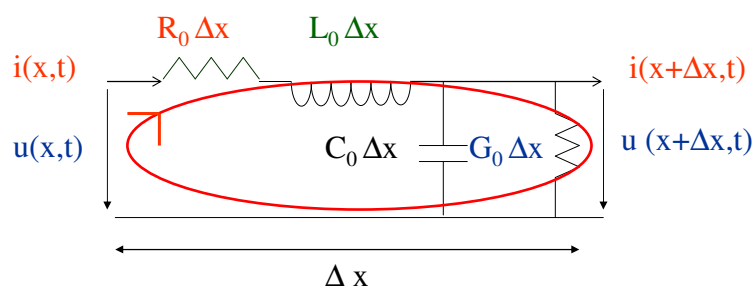
## Transmission line equations

Consider one segment at position  $x$  along the line:



- $R_0$ : the resistance of the conductors per unit length in  $\Omega/m$ ;
- $L_0$ : the inductance of the conductors per unit length in  $H/m$ ;
- $G_0$ : the conductance of the insulation medium per unit length in  $1/\Omega m$ ;
- $C_0$ : the capacitance of the conductors per unit length in  $F/m$ .

**Next Step:** To establish relations among the currents and the voltages at  $x$  and  $x + \Delta x$

**By application of KVL:**

$$-u(x,t) + u(x + \Delta x, t) + R_0 \cdot \Delta x \cdot i + L_0 \cdot \Delta x \cdot \frac{\partial i}{\partial t} = 0$$


**but:**

$$u(x + \Delta x, t) = u(x, t) + \frac{\partial u}{\partial x} \cdot \Delta x$$

**Divided by  $\Delta x$  and let  $\Delta x \rightarrow 0$**

$$-\frac{\partial u}{\partial x} = R_0 \cdot i + L_0 \cdot \frac{\partial i}{\partial t}$$

**First order telegrapher's equations**

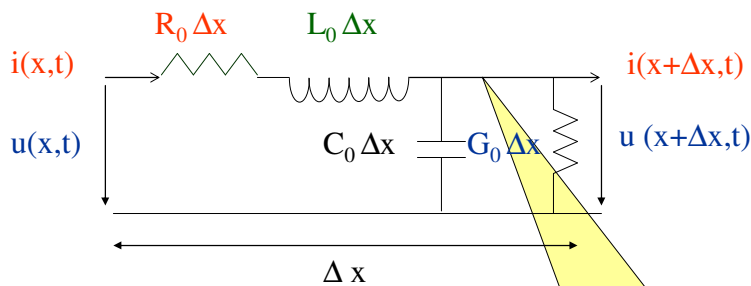

**By application of KCL**

$$-i(x,t) + i(x + \Delta x, t) + G_0 \cdot \Delta x \cdot u + C_0 \cdot \Delta x \cdot \frac{\partial u}{\partial t} = 0$$

$$i(x + \Delta x, t) = i(x, t) + \frac{\partial i}{\partial x} \cdot \Delta x$$

$$-\frac{\partial i}{\partial x} = G_0 \cdot u + C_0 \cdot \frac{\partial u}{\partial t}$$

**First order telegrapher's equations**

## Comments on the TL equations

$$-\frac{\partial u}{\partial x} = R_0 \cdot i + L_0 \cdot \frac{\partial i}{\partial t}$$

$$-\frac{\partial i}{\partial x} = G_0 \cdot u + C_0 \cdot \frac{\partial u}{\partial t}$$

- both equations, within the level of approximations, are partial differential equations (PDE) that governing the voltage and the current along the transmission lines.
- the line primary parameters  $R_0$ ,  $L_0$ ,  $G_0$ ,  $C_0$  are related to the physical properties of the transmission line and may be functions of position  $x$ .
- give the line parameters, solutions of the equations describe the voltage and the current along the transmission lines

## Second order telegrapher's equation

$$-\frac{\partial u}{\partial x} = R_0 \cdot i + L_0 \cdot \frac{\partial i}{\partial t}$$

$$-\frac{\partial i}{\partial x} = G_0 \cdot u + C_0 \cdot \frac{\partial u}{\partial t}$$

Assume  $R_0, L_0, G_0, C_0$  are all constants

$$-\frac{\partial^2 u}{\partial x^2} = R_0 \cdot \frac{\partial i}{\partial x} + L_0 \cdot \frac{\partial^2 i}{\partial t \cdot \partial x}$$

$$-\frac{\partial^2 i}{\partial t \cdot \partial x} = G_0 \cdot \frac{\partial u}{\partial t} + C_0 \cdot \frac{\partial^2 u}{\partial t^2}$$

$$-\frac{\partial^2 u}{\partial x^2} = R_0 \cdot \left( -G_0 \cdot u - C_0 \cdot \frac{\partial u}{\partial t} \right) + L_0 \cdot \left( -G_0 \cdot \frac{\partial u}{\partial t} - C_0 \cdot \frac{\partial^2 u}{\partial t^2} \right)$$

$$\frac{\partial^2 u}{\partial x^2} = R_0 \cdot G_0 \cdot u + (R_0 \cdot C_0 + G_0 \cdot L_0) \cdot \frac{\partial u}{\partial t} + L_0 \cdot C_0 \cdot \frac{\partial^2 u}{\partial t^2}$$

$$\frac{\partial^2 i}{\partial x^2} = R_0 \cdot G_0 \cdot i + (R_0 \cdot C_0 + G_0 \cdot L_0) \cdot \frac{\partial i}{\partial t} + L_0 \cdot C_0 \cdot \frac{\partial^2 i}{\partial t^2}$$

## Wave Equations for Lossless Transmission Line

If the line is lossless, then  $R_0 = G_0 = 0$ , therefore:

$$\frac{\partial^2 i}{\partial x^2} = L_0 \cdot C_0 \cdot \frac{\partial^2 i}{\partial t^2} = \frac{1}{v^2} \cdot \frac{\partial^2 i}{\partial t^2} \qquad \frac{\partial^2 u}{\partial x^2} = \frac{1}{v^2} \cdot \frac{\partial^2 u}{\partial t^2}$$

$$v = \frac{1}{\sqrt{L_0 \cdot C_0}}$$

The velocity of the propagating wave

**Conclusion:** The voltage and the current travel along the transmission line are governed by the wave equations

## Solutions of the Wave Equation for Lossless Transmission Line

$$u(x, t) = u_d \left( t - \frac{x}{v} \right) + u_i \left( t + \frac{x}{v} \right) \quad \text{Eq.1}$$


$$i(x, t) = i_d \left( t - \frac{x}{v} \right) + i_i \left( t + \frac{x}{v} \right) \quad \text{Eq.2}$$

$$u_d \left( t - \frac{x}{v} \right) \text{ and } i_d \left( t - \frac{x}{v} \right) \quad \text{Forward propagating wave}$$

$$u_i \left( t + \frac{x}{v} \right) \text{ and } i_i \left( t + \frac{x}{v} \right) \quad \text{Backward propagating wave}$$

**Conclusion:** The total voltage and the current are sum of the forward and the backward propagating waves along the transmission line as expressed in (1-2).

## Example: Forward Propagating Wave

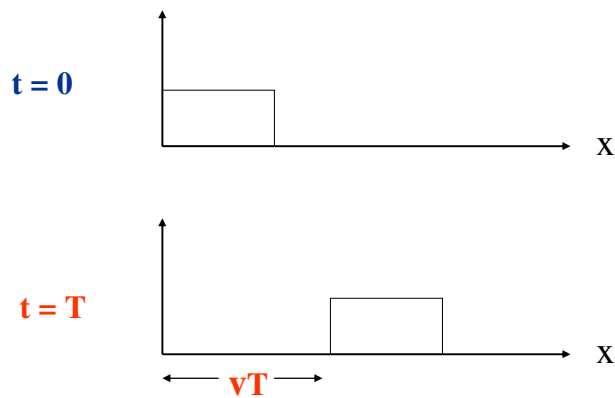

## Derivation of the Power Equation

Multiply eq. (1) by  $i(x,t)$  and eq. (2) by  $u(x,t)$ , add:

$$(1) \quad \frac{\partial u}{\partial x} = R_0 \cdot i + L_0 \cdot \frac{\partial i}{\partial t} \qquad (2) \quad \frac{\partial i}{\partial x} = G_0 \cdot u + C_0 \cdot \frac{\partial u}{\partial t}$$

$$-\frac{\partial u}{\partial x} \cdot i = R_0 \cdot i^2 + L_0 \cdot i \cdot \frac{\partial i}{\partial t} \qquad -\frac{\partial i}{\partial x} \cdot u = G_0 \cdot u^2 + C_0 \cdot u \cdot \frac{\partial u}{\partial t}$$

$$-\frac{\partial}{\partial x} (ui) = R_0 \cdot i^2 + G_0 \cdot u^2 + \frac{\partial}{\partial t} \left( \frac{L_0 \cdot i^2}{2} \right) + \frac{\partial}{\partial t} \left( \frac{C_0 \cdot u^2}{2} \right)$$

$$-\frac{\partial p}{\partial x} = p_d + \frac{\partial W}{\partial t}$$

$p = u \cdot i$  **Total Power**  
 $p = R_0 \cdot i^2 + G_0 \cdot u^2$  **Power Dissipation**  
 $W = \frac{1}{2} \cdot (L_0 \cdot i^2 + C_0 \cdot u^2)$  **Stored EM Energy**

**Net Power Flow = Power Dissipation + Change in Stored Energy!**

## Steady-State TL Equations

$$u(x, t) = U(x) \sqrt{2} \cdot \sin(\omega t + \gamma_u(x))$$

$$u(x, t) \Leftrightarrow \underline{U}(x) = U(x) \cdot e^{j \cdot \gamma_u}$$

$$i(x, t) = I(x) \sqrt{2} \cdot \sin(\omega t + \gamma_i(x))$$

$$i(x, t) \Leftrightarrow \underline{I}(x) = I(x) \cdot e^{j \cdot \gamma_i}$$

Real functions of x and t

Complex functions of x only

$\omega$  being the frequency of the sinusoidal signal

Furthermore:

$$\frac{\partial}{\partial x} u(x, t) \quad \text{or} \quad i(x, t) \Leftrightarrow \frac{d\underline{U}(x)}{dx} \quad \text{or} \quad \frac{d\underline{I}(x)}{dx}$$

$$\frac{\partial}{\partial t} u(x, t) \quad \text{or} \quad i(x, t) \Leftrightarrow j\omega \underline{U}(x) \quad \text{or} \quad \underline{I}(x)$$


$$-\frac{\partial u}{\partial x} = R_0 \cdot i + L_0 \cdot \frac{\partial i}{\partial t} \quad \Rightarrow \quad -\frac{d\underline{U}}{dx} = R_0 \cdot \underline{I} + j\omega L_0 \cdot \underline{I} = (R_0 + j\omega L_0) \cdot \underline{I}$$

$$-\frac{\partial i}{\partial x} = G_0 \cdot u + C_0 \cdot \frac{\partial u}{\partial t} \quad \Rightarrow \quad -\frac{d\underline{I}}{dx} = (G_0 + j\omega C_0) \cdot \underline{U}$$

### Comments on the steady-state TL equations

- Both equations are **ordinary differential equations (ODE)** governing the complex voltage and the current  $\underline{U}(x)$  and  $\underline{I}(x)$  along the TL.
- The complex  $\underline{U}(x)$  and  $\underline{I}(x)$  have no direct physical meaning. On the other hand, once the complex  $\underline{U}$  and  $\underline{I}$  are known, the physical time-dependent, real solutions can be obtained.
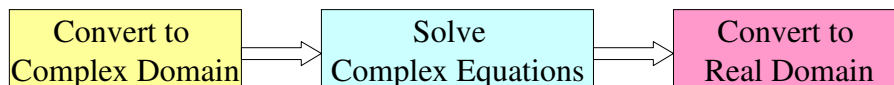
### Procedure for Sinusoidal Steady State Solutions



## Steady-state TL equations (cont)

$$-\frac{d\underline{U}}{dx} = (R_0 + j\omega L_0) \cdot \underline{I} \quad (4)$$

$$-\frac{d\underline{I}}{dx} = (G_0 + j\omega C_0) \cdot \underline{U} \quad (5)$$

If  $R_0, L_0, G_0, C_0$  are all constants of  $x$  (**homogeneous TL**), then by taking derivative of (4) and making use of (5), we have:

$$\frac{d\underline{U}^2}{dx^2} = (R_0 + j\omega L_0) \cdot (G_0 + j\omega C_0) \cdot \underline{U} \rightarrow \frac{d\underline{U}^2}{dx^2} - \underline{\gamma}^2 \cdot \underline{U} = 0$$

Similarly, we have:

$$\frac{d\underline{I}^2}{dx^2} = (R_0 + j\omega L_0) \cdot (G_0 + j\omega C_0) \cdot \underline{I} \rightarrow \frac{d\underline{I}^2}{dx^2} - \underline{\gamma}^2 \cdot \underline{I} = 0$$

$$\underline{\gamma} = \sqrt{(R_0 + j\omega L_0) \cdot (G_0 + j\omega C_0)}$$

**Complex propagation constant in 1/m**

$$\underline{\gamma} = \sqrt{(R_0 + j\omega L_0) \cdot (G_0 + j\omega C_0)} = \alpha + j\beta$$

$\alpha$  = attenuation constant


$$[\alpha]_{SI} = \frac{1 \text{ Neper}}{1 \text{ m}} = \frac{1 \text{ Np}}{1 \text{ m}}$$

$\beta$  = phase constant

$$[\beta] = \frac{1 \text{ rad}}{1 \text{ m}}$$

$\underline{Z}_0 = R_0 + j\omega L_0$  , longitudinal impedance

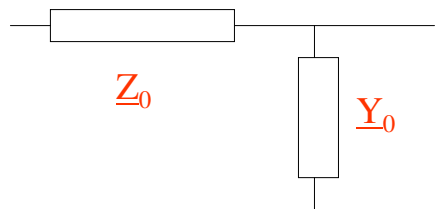$\underline{Y}_0 = G_0 + j\omega C_0$  , transversal admittances



The expression for the attenuation and phase constants with respect with the primary TL parameters

$$\alpha = \sqrt{\frac{1}{2}(Z_0 Y_0 + R_0 G_0 + \omega^2 L_0 C_0)}$$

$$\beta = \sqrt{\frac{1}{2}(Z_0 Y_0 + \omega^2 L_0 C_0 - R_0 G_0)}$$

Where  $Z_0$  and  $Y_0$  are:

$$Z_0 = \sqrt{R_0^2 + \omega^2 L_0^2}, \quad Y_0 = \sqrt{G_0^2 + \omega^2 C_0^2}$$

## General Solutions

$$\frac{d^2 \underline{U}}{dx^2} - \underline{\gamma}^2 \cdot \underline{U} = 0$$

$$\underline{U}(x) = \underline{A} \cdot e^{-\underline{\gamma} \cdot x} + \underline{B} \cdot e^{+\underline{\gamma} \cdot x}$$

$$\underline{U}(x) = \underline{U}_d + \underline{U}_i$$

$$-\frac{d\underline{U}}{dx} = (R_0 + j\omega L_0) \cdot \underline{I} = \underline{A} \cdot \underline{\gamma} \cdot e^{-\underline{\gamma}x} - \underline{B} \cdot \underline{\gamma} \cdot e^{+\underline{\gamma}x}$$

$$\underline{I} = \frac{1}{(R_0 + j\omega L_0)} \cdot (\underline{A} \cdot \underline{\gamma} \cdot e^{-\underline{\gamma}x} - \underline{B} \cdot \underline{\gamma} \cdot e^{+\underline{\gamma}x})$$

$$\underline{I} = \frac{\underline{\gamma}}{(R_0 + j\omega L_0)} \cdot (\underline{U}_d - \underline{U}_i) = \frac{1}{Z_c} \cdot (\underline{U}_d - \underline{U}_i) = \underline{I}_d - \underline{I}_i$$



### Physical Meaning of the General Solution:

- the total voltage/current are sum of the forward (exp[- $\gamma x$ ]) and the backward (exp[+ $\gamma x$ ]) propagating waves:

$$\underline{U}(x) = \underline{U}_d + \underline{U}_i$$

- the forward propagating voltage (or current) waves  $\underline{U}_d$  (or  $\underline{I}_d$ ) are also called the direct voltage (or current) waves;
- the backward propagating voltage (or current) waves  $\underline{U}_i$  (or  $\underline{I}_i$ ) are also called the inverse voltage (or current) waves;

### Relationship between $\underline{U}_d$ , $\underline{U}_i$ and $\underline{I}_d$ , $\underline{I}_i$

$$\frac{\underline{U}_d}{\underline{I}_d} = -\frac{\underline{U}_i}{\underline{I}_i} = \sqrt{\frac{R_0 + j\omega L_0}{G_0 + j\omega C_0}} = \underline{Z}_c$$

$\underline{Z}_c$ : the characteristic impedance of the transmission line ( $\Omega$ )

### The secondary TL parameters

#### Complex propagation constant

$$\gamma = \sqrt{(R_0 + j\omega L_0) \cdot (G_0 + j\omega C_0)}$$

#### Characteristic impedance ( $\Omega$ )

$$\underline{Z}_c = \sqrt{\frac{R_0 + j\omega L_0}{G_0 + j\omega C_0}} = \sqrt{\frac{\underline{Z}_0}{\underline{Y}_0}}$$

Where:


- $\underline{Z}_0$  is the longitudinal impedance
- $\underline{Y}_0$  is the transversal admittance

$$\underline{U}(x) = \underline{A} \cdot e^{-\gamma \cdot x} + \underline{B} \cdot e^{+\gamma \cdot x}$$

Only two knowns  $\underline{A}$  and  $\underline{B}$  remain to be determined!

## Equivalent TL equations

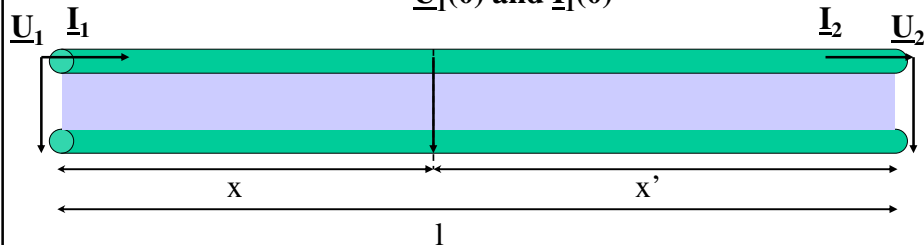1) Suppose that the voltage and the current for  $x = 0$  are known:  
 $\underline{U}_1(0)$  and  $\underline{I}_1(0)$



$$\underline{U}(0) = A \cdot e^{-\gamma \cdot x} + B \cdot e^{+\gamma \cdot x} = A + B = \underline{U}_1$$

$$\underline{I}(0) = \frac{1}{\underline{Z}_c} \cdot (A \cdot e^{-\gamma \cdot x} - B \cdot e^{+\gamma \cdot x}) = \frac{1}{\underline{Z}_c} \cdot (A - B) = \underline{I}_1$$

$$A + B = \underline{U}_1$$

$$A - B = \underline{Z}_c \cdot \underline{I}_1$$



$$A = \frac{\underline{U}_1 + \underline{I}_1 \cdot \underline{Z}_c}{2}$$

$$B = \frac{\underline{U}_1 - \underline{I}_1 \cdot \underline{Z}_c}{2}$$

**Finally:**

$$\underline{U}(x) = \left( \frac{\underline{U}_1 + \underline{I}_1 \cdot \underline{Z}_c}{2} \right) \cdot e^{-\gamma \cdot x} + \left( \frac{\underline{U}_1 - \underline{I}_1 \cdot \underline{Z}_c}{2} \right) \cdot e^{+\gamma \cdot x}$$


$$\underline{I}(x) = \frac{1}{\underline{Z}_c} \left\{ \left( \frac{\underline{U}_1 + \underline{I}_1 \cdot \underline{Z}_c}{2} \right) \cdot e^{-\gamma \cdot x} - \left( \frac{\underline{U}_1 - \underline{I}_1 \cdot \underline{Z}_c}{2} \right) \cdot e^{+\gamma \cdot x} \right\}$$

$$U(x) = U_1 \cdot ch(\underline{\gamma} \cdot x) - I_1 \cdot Z_c \cdot sh(\underline{\gamma} \cdot x)$$

$$I(x) = I_1 \cdot ch(\underline{\gamma} \cdot x) - U_1 \cdot \frac{1}{Z_c} \cdot sh(\underline{\gamma} \cdot x)$$

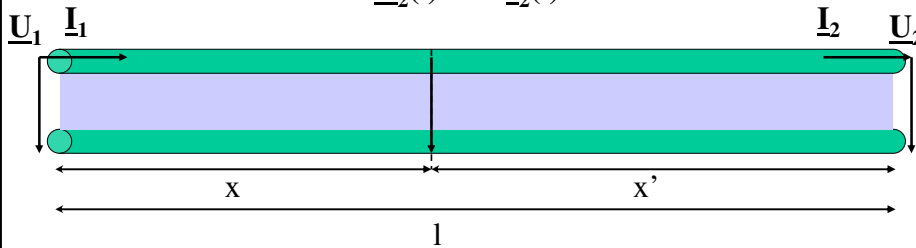2) Suppose that the voltage and the current for  $x = l$  are known

$\underline{U}_2(l)$  and  $\underline{I}_2(l)$




$$U(x') = U_2 \cdot ch(\underline{\gamma} \cdot x') + I_2 \cdot Z_c \cdot sh(\underline{\gamma} \cdot x')$$

$$I(x') = I_2 \cdot ch(\underline{\gamma} \cdot x') + U_2 \cdot \frac{1}{Z_c} \cdot sh(\underline{\gamma} \cdot x')$$

**Very important equations !!**

**Input impedance of a TL**

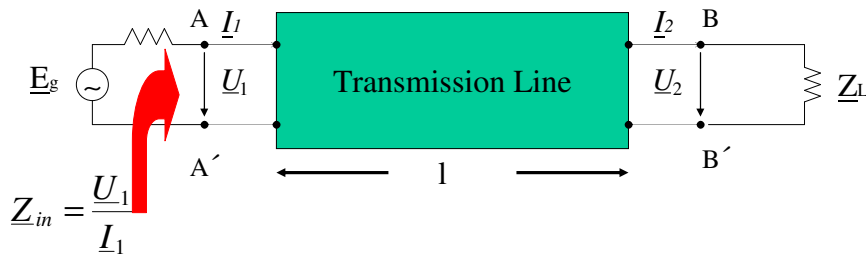

$$\underline{Z}_{in}(x'=l) = \frac{\underline{U}_1}{\underline{I}_1} = \frac{\underline{U}_2 \cdot \text{ch}(\underline{\gamma} \cdot l) + \underline{I}_2 \cdot \underline{Z}_C \cdot \text{sh}(\underline{\gamma} \cdot l)}{\underline{I}_2 \cdot \text{ch}(\underline{\gamma} \cdot l) + \underline{U}_2 \cdot \frac{1}{\underline{Z}_C} \cdot \text{sh}(\underline{\gamma} \cdot l)}$$

Supposing the external impedance:  $\underline{Z}_L = \frac{\underline{U}_2}{\underline{I}_2}$

$$\underline{Z}_{in} = \frac{\underline{Z}_L \cdot \text{ch}(\underline{\gamma} \cdot l) + \underline{Z}_C \cdot \text{sh}(\underline{\gamma} \cdot l)}{\text{ch}(\underline{\gamma} \cdot l) + \frac{\underline{Z}_L}{\underline{Z}_C} \cdot \text{sh}(\underline{\gamma} \cdot l)} = \underline{Z}_C \cdot \frac{\underline{Z}_L \cdot \text{ch}(\underline{\gamma} \cdot l) + \underline{Z}_C \cdot \text{sh}(\underline{\gamma} \cdot l)}{\underline{Z}_C \cdot \text{ch}(\underline{\gamma} \cdot l) + \underline{Z}_L \cdot \text{sh}(\underline{\gamma} \cdot l)}$$

Particular cases for the input impedances:

a) TL in short circuit:  $\underline{Z}_L \rightarrow 0$   $\underline{Z}_{in}^0 = \underline{Z}_C \cdot \frac{\text{sh}(\underline{\gamma} \cdot l)}{\text{ch}(\underline{\gamma} \cdot l)} = \underline{Z}_C \cdot \text{th}(\underline{\gamma} \cdot l)$

b) TL in open circuit:  $\underline{Z}_L \rightarrow \infty$   $\underline{Z}_{in}^{sc} = \underline{Z}_C \cdot \frac{\text{ch}(\underline{\gamma} \cdot l)}{\text{sh}(\underline{\gamma} \cdot l)} = \underline{Z}_C \cdot \frac{1}{\text{th}(\underline{\gamma} \cdot l)}$

If we take into account both particular cases:

$$\underline{Z}_{in}^0 \cdot \underline{Z}_{in}^{sc} = \underline{Z}_C^2 \Rightarrow \underline{Z}_C = \sqrt{\underline{Z}_{in}^0 \cdot \underline{Z}_{in}^{sc}}$$

$$\frac{\underline{Z}_{in}^0}{\underline{Z}_{in}^{sc}} = (\text{th}(\underline{\gamma} \cdot l))^2 \Rightarrow \underline{\gamma} \cdot l = \arg \text{th} \sqrt{\frac{\underline{Z}_{in}^0}{\underline{Z}_{in}^{sc}}}$$

$$\underline{\gamma} = \alpha + \beta j = \frac{1}{l} \cdot \arg \text{th} \sqrt{\frac{\underline{Z}_{in}^0}{\underline{Z}_{in}^{sc}}}$$

c) TL closed on the characteristic impedance:  $\underline{Z}_L = \underline{Z}_C$

$$\underline{Z}_{in} = \underline{Z}_C \cdot \frac{\underline{Z}_C \cdot \text{ch}(\underline{\gamma} \cdot l) + \underline{Z}_C \cdot \text{sh}(\underline{\gamma} \cdot l)}{\underline{Z}_C \cdot \text{ch}(\underline{\gamma} \cdot l) + \underline{Z}_C \cdot \text{sh}(\underline{\gamma} \cdot l)} = \underline{Z}_C$$

## Lossless Transmission Line

If the line is lossless, then  $R_0 = G_0 = 0$ , therefore:

$$\underline{Z}_c = \sqrt{\frac{R_0 + j\omega L_0}{G_0 + j\omega C_0}} = \sqrt{\frac{L_0}{C_0}} = \text{real ( pure resistive )}$$

$$\underline{\gamma} = \sqrt{(R_0 + j\omega L_0) \cdot (G_0 + j\omega C_0)} = j\omega \sqrt{L_0 \cdot C_0}$$

$$\underline{\gamma} = \alpha + j\beta = j\omega \sqrt{L_0 \cdot C_0}$$

$$\alpha = 0$$

$$\beta = \omega \sqrt{L_0 \cdot C_0} = 2\pi f \sqrt{L_0 \cdot C_0} = \frac{2\pi}{v} \cdot f = \frac{2\pi}{v} \cdot \frac{1}{T} = \frac{2\pi}{\lambda}$$

Where  $v$  is the velocity of the wave:

$$v = \frac{1}{\sqrt{L_0 \cdot C_0}}$$

## The input impedance of a lossless TL

$$\underline{Z}_{in} = \underline{Z}_c \cdot \frac{\underline{Z}_L \cdot \text{ch}(\underline{\gamma} \cdot l) + \underline{Z}_c \cdot \text{sh}(\underline{\gamma} \cdot l)}{\underline{Z}_c \cdot \text{ch}(\underline{\gamma} \cdot l) + \underline{Z}_L \cdot \text{sh}(\underline{\gamma} \cdot l)}$$

$$\begin{aligned} \text{ch}(\underline{\gamma} \cdot l) &= \text{ch}(j \cdot \beta \cdot l) = \cos(\beta \cdot l) \\ \text{sh}(\underline{\gamma} \cdot l) &= \text{sh}(j \cdot \beta \cdot l) = j \cdot \sin(\beta \cdot l) \end{aligned}$$

$$\underline{Z}_{in} = \sqrt{\frac{L_0}{C_0}} \cdot \frac{\underline{Z}_L \cdot \cos(\beta \cdot l) + \underline{Z}_c \cdot j \cdot \sin(\beta \cdot l)}{\underline{Z}_c \cdot \cos(\beta \cdot l) + \underline{Z}_L \cdot j \cdot \sin(\beta \cdot l)}$$

**Particular cases:**

a) The length of the TL is equal with a quarter of the wave length:

$$l = \frac{\lambda}{4}$$

$$\underline{Z}_{in} = \sqrt{\frac{L_0}{C_0}} \cdot \frac{\underline{Z}_L \cdot \cos(\beta \cdot \frac{\lambda}{4}) + \underline{Z}_C \cdot j \cdot \sin(\beta \cdot \frac{\lambda}{4})}{\underline{Z}_C \cdot \cos(\beta \cdot \frac{\lambda}{4}) + \underline{Z}_L \cdot j \cdot \sin(\beta \cdot \frac{\lambda}{4})}$$

$$\beta = \omega \sqrt{L_0 \cdot C_0} = 2\pi f \sqrt{L_0 \cdot C_0} = \frac{2\pi}{v} \cdot \frac{1}{T} = \frac{2\pi}{\lambda} \Rightarrow \beta \cdot \lambda = 2\pi$$

$$\underline{Z}_{in} = \sqrt{\frac{L_0}{C_0}} \cdot \frac{\underline{Z}_L \cdot \cos(\frac{\pi}{2}) + \underline{Z}_C \cdot j \cdot \sin(\frac{\pi}{2})}{\underline{Z}_C \cdot \cos(\frac{\pi}{2}) + \underline{Z}_L \cdot j \cdot \sin(\frac{\pi}{2})} = \sqrt{\frac{L_0}{C_0}} \cdot \frac{\underline{Z}_C \cdot j}{\underline{Z}_L \cdot j} = \frac{L_0}{C_0} \cdot \frac{1}{\underline{Z}_L}$$

If,  $\underline{Z}_L$  = inductive  $\underline{Z}_{in}$  will be capacitive and

$\underline{Z}_L$  = capacitive  $\underline{Z}_{in}$  will be inductive

- So, that a lossless TL having the length equal with a quarter of the wave length will act as a impedance transformer

#### Particular cases:

b) The length of the TL is equal with a half of the wave length:


$$l = \frac{\lambda}{2}$$

$$\underline{Z}_{in} = \sqrt{\frac{L_0}{C_0}} \cdot \frac{\underline{Z}_L \cdot \cos(\beta \cdot l) + \underline{Z}_C \cdot j \cdot \sin(\beta \cdot l)}{\underline{Z}_C \cdot \cos(\beta \cdot l) + \underline{Z}_L \cdot j \cdot \sin(\beta \cdot l)} \quad \beta \cdot \lambda = 2\pi$$

$$\underline{Z}_{in} = \sqrt{\frac{L_0}{C_0}} \cdot \frac{\underline{Z}_L \cdot \cos(\pi) + \underline{Z}_C \cdot j \cdot \sin(\pi)}{\underline{Z}_C \cdot \cos(\pi) + \underline{Z}_L \cdot j \cdot \sin(\pi)} = \sqrt{\frac{L_0}{C_0}} \cdot \frac{\underline{Z}_L}{\underline{Z}_C} = \underline{Z}_L$$

- So, that a lossless TL having the length equal with a half of the wave length will act as a impedance adaptor

## Semi-Infinite Line

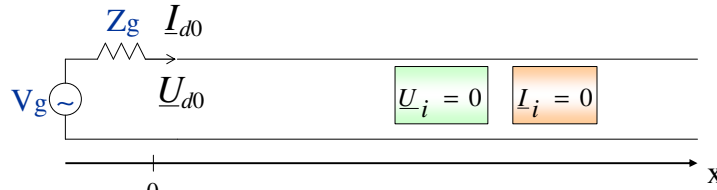

Suppose that the line extends to infinite along + x. Therefore, the backward propagating waves do not exist. We obtain:

$$\underline{U}(x) = \underline{U}_d + \underline{U}_i$$

$$\underline{I} = \frac{1}{\underline{Z}_c} \cdot (\underline{U}_d - \underline{U}_i) = \underline{I}_d - \underline{I}_i$$

$$\underline{U}(x) = \underline{U}_d = A \cdot e^{-\gamma \cdot x}$$

$$\underline{I}_d = \frac{\underline{U}_d}{\underline{Z}_c}$$

$\gamma$  is complex so that:


$$\underline{U}_d(x) = \underline{U}_{d0} \cdot e^{-\underline{\gamma} \cdot x} = U_{d0} \cdot e^{j \cdot \gamma_{d0} \cdot x} \cdot e^{-\alpha \cdot x - j \cdot \beta \cdot x}$$

$$\underline{U}_d(x) = \underline{U}_{d0} \cdot e^{-\underline{\gamma} \cdot x} = U_{d0} \cdot e^{j \cdot \gamma_{d0} \cdot x} \cdot e^{-\alpha \cdot x - j \cdot \beta \cdot x}$$

The instantaneous direct voltage and current are

$$u_d(x,t) = U_{d0} \cdot \sqrt{2} \cdot e^{-\alpha \cdot x} \cdot \sin(\omega t - \beta \cdot x + \gamma_{d0})$$
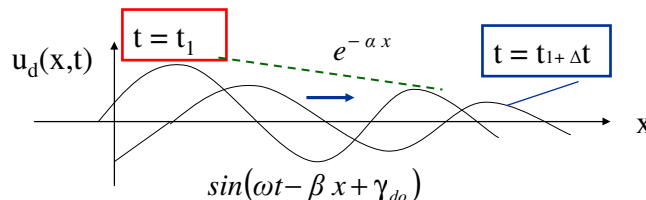
$$i_d(x,t) = I_{d0} \cdot \sqrt{2} \cdot e^{-\alpha \cdot x} \cdot \sin(\omega t - \beta \cdot x + \gamma_{d0} + \vartheta)$$



**Amplitude:** decay according to  $\exp(-\alpha x)$ , therefore  $\alpha$  is the amplitude decay constant of the wave

### The instantaneous inverse voltage and current:

$$u_i(x, t) = U_{i0} \cdot \sqrt{2} \cdot e^{\alpha \cdot x} \cdot \sin(\omega t + \beta \cdot x + \gamma_{i0})$$

$$i_i(x, t) = I_{i0} \cdot \sqrt{2} \cdot e^{\alpha \cdot x} \cdot \sin(\omega t + \beta \cdot x + \gamma_{i0} + \vartheta_i)$$

$$\frac{d}{dt}(\omega t + \beta x + \gamma_{i0}) = 0 \quad \longrightarrow \quad v_i = -\frac{dx}{dt} = -\frac{\omega}{\beta} = v_d$$

**Amplitude:** decay according to  $\exp(\alpha x)$ , therefore  $\alpha$  is the amplitude decay constant of the wave

## Phase Velocity

**Definition:** The velocity at which the phase of the wave travels

Let us observe a point of constant phase such that:

$$\omega t - \beta x = \text{const}$$

Take derivative with respect to time t:  $\omega - \beta \frac{dx}{dt} = 0$

Re-arrange so that that phase velocity is expressed as:

$$v_d = \frac{dx}{dt} = \frac{\omega}{\beta}$$

- which is a function of frequency and dependent on the physical properties of the transmission line through  $\beta$ .



## Heaviside TL conditions

If:  $\frac{R_0}{L_0} = \frac{G_0}{C_0}$   $\rightarrow$   $\underline{\gamma} = \sqrt{(R_0 + j\omega L_0) \cdot (G_0 + j\omega C_0)}$

$$\underline{\gamma} = \sqrt{R_0 \cdot G_0 \cdot \left(1 + \frac{j\omega L_0}{R_0}\right) \cdot \left(1 + \frac{j\omega C_0}{G_0}\right)} = \sqrt{R_0 \cdot G_0 \cdot \left(1 + \frac{j\omega L_0}{R_0}\right)^2} =$$

$$= \left(1 + \frac{j\omega L_0}{R_0}\right) \cdot \sqrt{R_0 \cdot G_0} = \sqrt{R_0 \cdot G_0} + j\omega L_0 \cdot \sqrt{\frac{G_0}{R_0}} = \sqrt{R_0 \cdot G_0} + j\omega \sqrt{L_0 \cdot C_0}$$

$$\alpha = \sqrt{R_0 \cdot G_0}$$

$$\beta = \omega \sqrt{L_0 \cdot C_0}$$

**Important !!!!**

## Heaviside TL conditions

$$\alpha = \sqrt{R_0 \cdot G_0}$$

$$\beta = \omega \sqrt{L_0 \cdot C_0}$$

$$v_d = \frac{\omega}{\beta}$$

$$v_d = \frac{\omega}{\beta} = \frac{\omega}{\omega \sqrt{L_0 \cdot C_0}} = \frac{1}{\sqrt{L_0 \cdot C_0}} \quad (\text{independent of } f)$$

**TL without distortions !!!!**